

**22bec121**

**Experiment – 5**

**Date:-15/2/2024**

**Lab Work**

**Q1 .Post Lab Exercises**

**Code (Generated)**

```
module snehexp5(  
    Mode,  
    CLK,  
    HIGH,  
    Q3,  
    Q2,  
    Q1,  
    Q0  
);
```

```
input wire    Mode;  
input wire    CLK;  
input wire    HIGH;  
output reg    Q3;  
output wire    Q2;  
output wire    Q1;  
output wire    Q0;
```

```
wire    SYNTHESIZED_WIRE_0;  
wire    SYNTHESIZED_WIRE_1;
```

```
wire    SYNTHESIZED_WIRE_2;
```

```
reg     JKFF_A;
```

```
reg     JKFF_2;
```

```
reg     JKFF_3;
```

```
assign  Q2 = JKFF_3;
```

```
assign  Q1 = JKFF_2;
```

```
assign  Q0 = JKFF_A;
```

```
always@(posedge SYNTHESIZED_WIRE_0)
```

```
begin
```

```
    JKFF_2 <= ~JKFF_2 & HIGH | JKFF_2 & ~HIGH;
```

```
end
```

```
always@(posedge SYNTHESIZED_WIRE_1)
```

```
begin
```

```
    JKFF_3 <= ~JKFF_3 & HIGH | JKFF_3 & ~HIGH;
```

```
end
```

```
always@(posedge SYNTHESIZED_WIRE_2)
```

```
begin
```

```
    Q3 <= ~Q3 & HIGH | Q3 & ~HIGH;
```

```
end
```

```
always@(posedge CLK)
```

```
begin
    JKFF_A <= ~JKFF_A & HIGH | JKFF_A & ~HIGH;
end

assign SYNTHESIZED_WIRE_0 = Mode ^ JKFF_A;

assign SYNTHESIZED_WIRE_1 = Mode ^ JKFF_2;

assign SYNTHESIZED_WIRE_2 = Mode ^ JKFF_3;
endmodule
```

Quartus II 64-Bit - D:/22bec121/snehexp5 - snehexp5

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

snehexp5

Project Navigator snehexp5.bdf Compilation Report - snehexp5 snehexp5.v

Cydone II: EP2C35F67

snehexp5

Hierarchy

Tasks

Flow: Customize...

```
1 module snehexp5(  
2     Mode,  
3     CLK,  
4     HIGH,  
5     Q3,  
6     Q2,  
7     Q1,  
8     Q0  
9 );  
10  
11  
12 input wire Mode;  
13 input wire CLK;  
14 input wire HIGH;  
15 output reg Q3;  
16 output wire Q2;  
17 output wire Q1;  
18 output wire Q0;  
19  
20 wire SYNTHESIZED_WIRE_0;  
21 wire SYNTHESIZED_WIRE_1;  
22 wire SYNTHESIZED_WIRE_2;  
23 reg JKFF_A;  
24 reg JKFF_2;  
25 reg JKFF_3;  
26  
27 assign Q2 = JKFF_3;  
28 assign Q1 = JKFF_2;  
29 assign Q0 = JKFF_A;  
30  
31
```

Compile Des  
Analysis  
Edit Se  
View R  
Analys  
Partitic  
Netlist  
RT  
Str

All

Message

Running Quartus II 64-Bit Create Verilog File

System Processing (6)

1008, 0 100% 00:00:01

Quartus II 64-Bit - D:/22bec121/snehexp5 - snehexp5

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

snehexp5

Project Navigator

snehexp5.bdf

Compilation Report - snehexp5

snehexp5.v

Cyclone II: EP2C35F67

snehexp5

```

30
31 always@(posedge SYNTHESIZED_WIRE_0)
32 begin
33     JKFF_2 <= ~JKFF_2 & HIGH | JKFF_2 & ~HIGH;
34 end
35
36
37 always@(posedge SYNTHESIZED_WIRE_1)
38 begin
39     JKFF_3 <= ~JKFF_3 & HIGH | JKFF_3 & ~HIGH;
40 end
41
42
43 always@(posedge SYNTHESIZED_WIRE_2)
44 begin
45     Q3 <= ~Q3 & HIGH | Q3 & ~HIGH;
46 end
47
48
49 always@(posedge CLK)
50 begin
51     JKFF_A <= ~JKFF_A & HIGH | JKFF_A & ~HIGH;
52 end
53
54 assign SYNTHESIZED_WIRE_0 = Mode ^ JKFF_A;
55
56 assign SYNTHESIZED_WIRE_1 = Mode ^ JKFF_2;
57
58 assign SYNTHESIZED_WIRE_2 = Mode ^ JKFF_3;
59 endmodule
60

```

Hierarchy

Tasks

How: ( Customize...

Compile Des

Analysis

Edit Se

View R

Analys

Partitt

Netlist

RT

Str

All

Message

Running Quartus II 64-Bit Create Verilog File

System Processing (6)

Ln 58 Col 45 Verilog HDL File 100% 00:00:01

## Block Design

Quartus II 64-Bit - D:/22bec121/snehexp5 - snehexp5

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

snehexp5

Project Navigator

snehexp5.bdf

Compilation Report - snehexp5

snehexp5.v

Cyclone II: EP2C35F67

snehexp5

Hierarchy

Tasks

Flow: C Customize...

Compile Des

Analysis I

Edit Se

View R

Analysis

Partitic

Netlist

RT

Stz

Mode

HIGH

CLK

FF1

FF2

FF3

FF4

Q0

Q1

Q2

Q3

Messages

All


TD Message

Running Quartus II 64-Bit Create Verilog File

System Processing (6)

1010,439 100% 00:00:01

## Output 1)Cyclone II (RTL View)

 

## 2)Cyclone II (TTL View)





**This is a tedious way to implement a circuit but it is a way to develop small circuits with ease .**

**We also generated Verilog Code from the Block Diagram to implement a 4 bit Up/Dow Counter .**