

22bec121

Experiment – 2

Date:-25/1/2024

Lab Work

Q1 . Write down the code for 1-bit full adder using behavioural style of modelling .

Code

```
module sneh20(input a,b,cin,output reg sum,cout);
```

```
always@(*)
```

```
begin
```

```
    case({a,b,cin})
```

```
        3'b000: begin sum=0;cout=0; end
```

```
        3'b001: begin sum=1;cout=0; end
```

```
        3'b010: begin sum=1;cout=0 ;end
```

```
        3'b011: begin sum=0;cout=1 ;end
```

```
        3'b100: begin sum=1;cout=0 ;end
```

```
        3'b101: begin sum=0;cout=1 ;end
```

```
        3'b110: begin sum=0;cout=1; end
```

```
        3'b111: begin sum=1;cout=1; end
```

```
    endcase
```

```
end
```



```
endmodule
```

```

1 //Case Statements
2 module sneh20(input a,b,cin,output reg sum,cout);
3
4 always@(*)
5 begin
6     case({a,b,cin})
7         3'b000: begin sum=0;cout=0; end
8         3'b001: begin sum=1;cout=0; end
9         3'b010: begin sum=1;cout=0 ;end
10        3'b011: begin sum=0;cout=1 ;end
11        3'b100: begin sum=1;cout=0 ;end
12        3'b101: begin sum=0;cout=1 ;end
13        3'b110: begin sum=0;cout=1; end
14        3'b111: begin sum=1;cout=1; end
15    endcase
16 end
17
18 endmodule
19

```

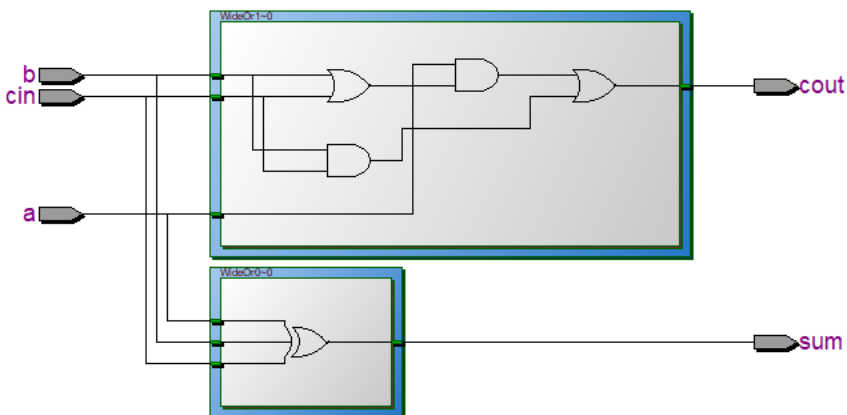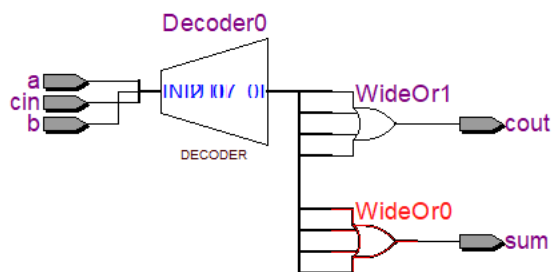
Output 1)Cyclone II (RTL View), 2) Cyclone II (TTL View)



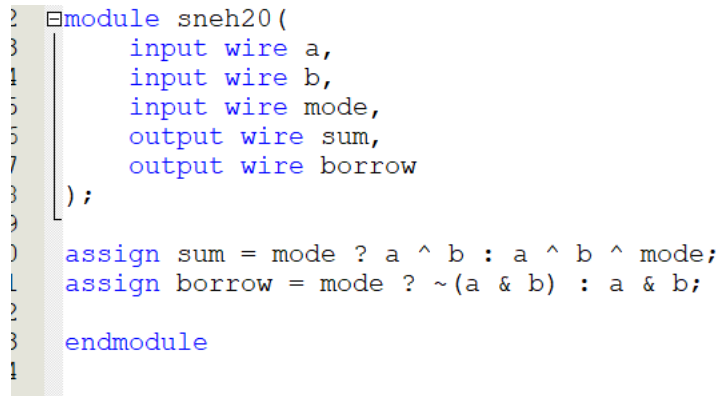Q2 . Modify the code that can perform Addition and Subtraction operation using a 'Mode Control Switch'.


Code


```
module sneh20(  
    input wire a,  
    input wire b,  
    input wire mode,  
    output wire sum,  
    output wire borrow  
);  
  
assign sum = mode ? a ^ b : a ^ b ^ mode;  
assign borrow = mode ? ~(a & b) : a & b;  
  
endmodule
```



Output

 1)Cyclone II (RTL View), 2) Cyclone II (TTL View)



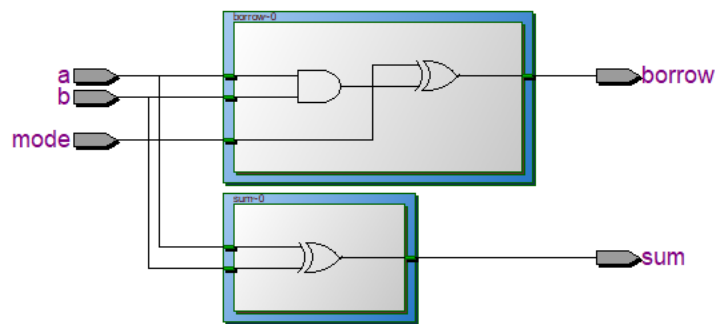

Code

```

module sneh20(

    input a,

    input b,

    input mode,

    output reg sum,

    output reg borrow

);

always @(*) begin

    if (mode == 0) begin

```

sum = a + b;

borrow = 0;

end else begin

sum = a - b;

borrow = (a < b) ? 1 : 0;

end



end

endmodule

```
35 module sneh20(  
36     input a,  
37     input b,  
38     input mode,  
39     output reg sum,  
40     output reg borrow  
41 );  
42  
43 always @(*) begin  
44     if (mode == 0) begin  
45         sum = a + b;  
46         borrow = 0;  
47     end else begin  
48         sum = a - b;  
49         borrow = (a < b) ? 1 : 0;  
50     end  
51 end  
52  
53 endmodule  
54
```

Output

 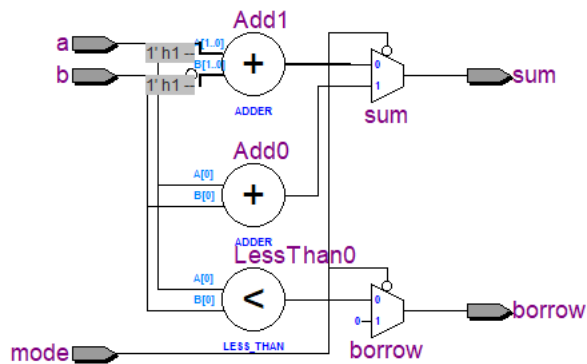1)Cyclone II (RTL View), 2) Cyclone II (TTL View)



Q3 . Carry out the modelling using If-Else-Else , Nested If .

Code

```
module sneh20(input a, b, cin, output reg sum, cout);
```

```
always @(*) begin
```

```
    if ({a, b, cin} == 3'b000) begin
```

```
        sum = 0;
```

```
        cout = 0;
```

```
    end else if ({a, b, cin} == 3'b001) begin
```

```
    sum = 1;

    cout = 0;

end else if ({a, b, cin} == 3'b010) begin

    sum = 1;

    cout = 0;

end else if ({a, b, cin} == 3'b011) begin

    sum = 0;

    cout = 1;

end else if ({a, b, cin} == 3'b100) begin

    sum = 1;

    cout = 0;

end else if ({a, b, cin} == 3'b101) begin

    sum = 0;

    cout = 1;

end else if ({a, b, cin} == 3'b110) begin

    sum = 0;

    cout = 1;

end else begin

    sum = 1;
```

cout = 1;


end


end

endmodule

```
56 module sneh20(input a, b, cin, output reg sum, cout);
57
58 always @(*) begin
59     if ({a, b, cin} == 3'b000) begin
60         sum = 0;
61         cout = 0;
62     end else if ({a, b, cin} == 3'b001) begin
63         sum = 1;
64         cout = 0;
65     end else if ({a, b, cin} == 3'b010) begin
66         sum = 1;
67         cout = 0;
68     end else if ({a, b, cin} == 3'b011) begin
69         sum = 0;
70         cout = 1;
71     end else if ({a, b, cin} == 3'b100) begin
72         sum = 1;
73         cout = 0;
74     end else if ({a, b, cin} == 3'b101) begin
75         sum = 0;
76         cout = 1;
77     end else if ({a, b, cin} == 3'b110) begin
78         sum = 0;
79         cout = 1;
80     end else begin
81         sum = 1;
82         cout = 1;
83     end
84 end
85
86 endmodule
```

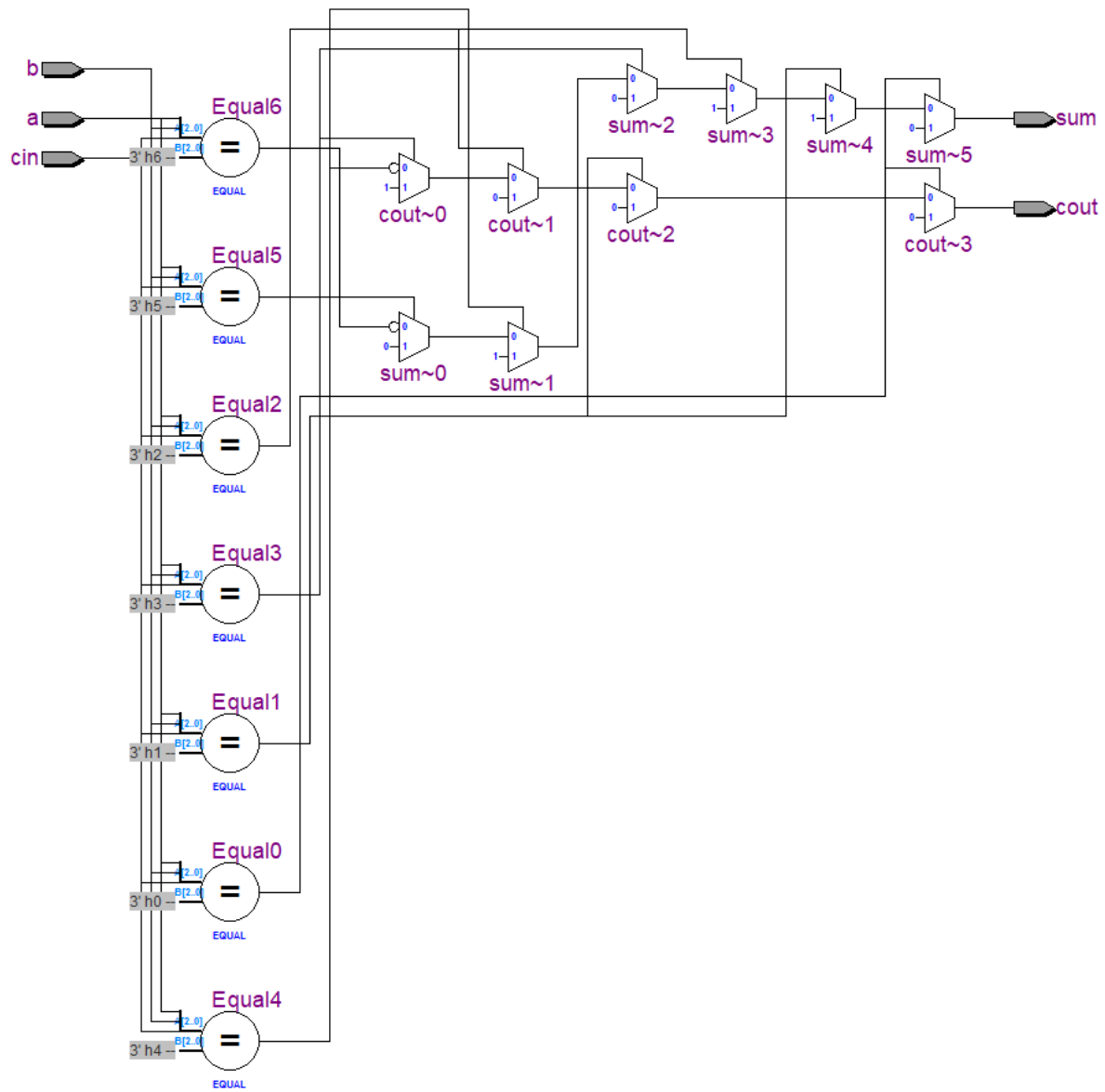
Output 1)Cyclone II (RTL View), 2) Cyclone II (TTL View)



 

Code

```
module sneh20(input a, b, cin, output reg sum, cout);
```

```
always @(*) begin
```

```
    if (a == 0) begin
```

```
        if (b == 0) begin
```

```
            if (cin == 0) begin
```

```
                sum = 0;
```

```
        cout = 0;
    end else begin
        sum = 1;
        cout = 0;
    end
end else begin
    if (cin == 0) begin
        sum = 1;
        cout = 0;
    end else begin
        sum = 0;
        cout = 1;
    end
end
end else begin
    if (b == 0) begin
        if (cin == 0) begin
            sum = 1;
            cout = 0;
        end else begin
            sum = 0;
            cout = 1;
        end
    end
end else begin
    if (cin == 0) begin
        sum = 0;
        cout = 1;
    end else begin
```



```
        sum = 1;
        cout = 1;
    end
end
end
end
```

endmodule

```
89 module sneh20(input a, b, cin, output reg sum, cout);
90
91 always @(*) begin
92     if (a == 0) begin
93         if (b == 0) begin
94             if (cin == 0) begin
95                 sum = 0;
96                 cout = 0;
97             end else begin
98                 sum = 1;
99                 cout = 0;
100             end
101         end else begin
102             if (cin == 0) begin
103                 sum = 1;
104                 cout = 0;
105             end else begin
106                 sum = 0;
107                 cout = 1;
108             end
109         end
110     end else begin
111         if (b == 0) begin
112             if (cin == 0) begin
113                 sum = 1;
114                 cout = 0;
115             end else begin
116                 sum = 0;
117                 cout = 1;
118             end
119         end
120     end
121 end
```

```
116         sum = 0;
117         cout = 1;
118     end
119 end else begin
120     if (cin == 0) begin
121         sum = 0;
122         cout = 1;
123     end else begin
124         sum = 1;
125         cout = 1;
126     end
127 end
128 end
129 end
130
131 endmodule
132
```

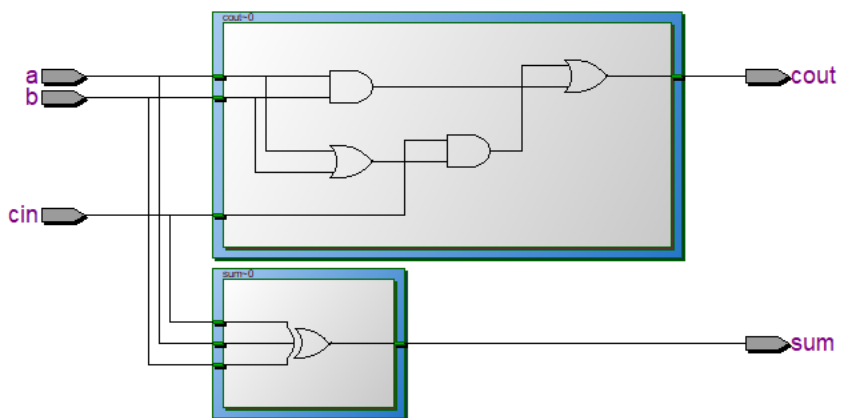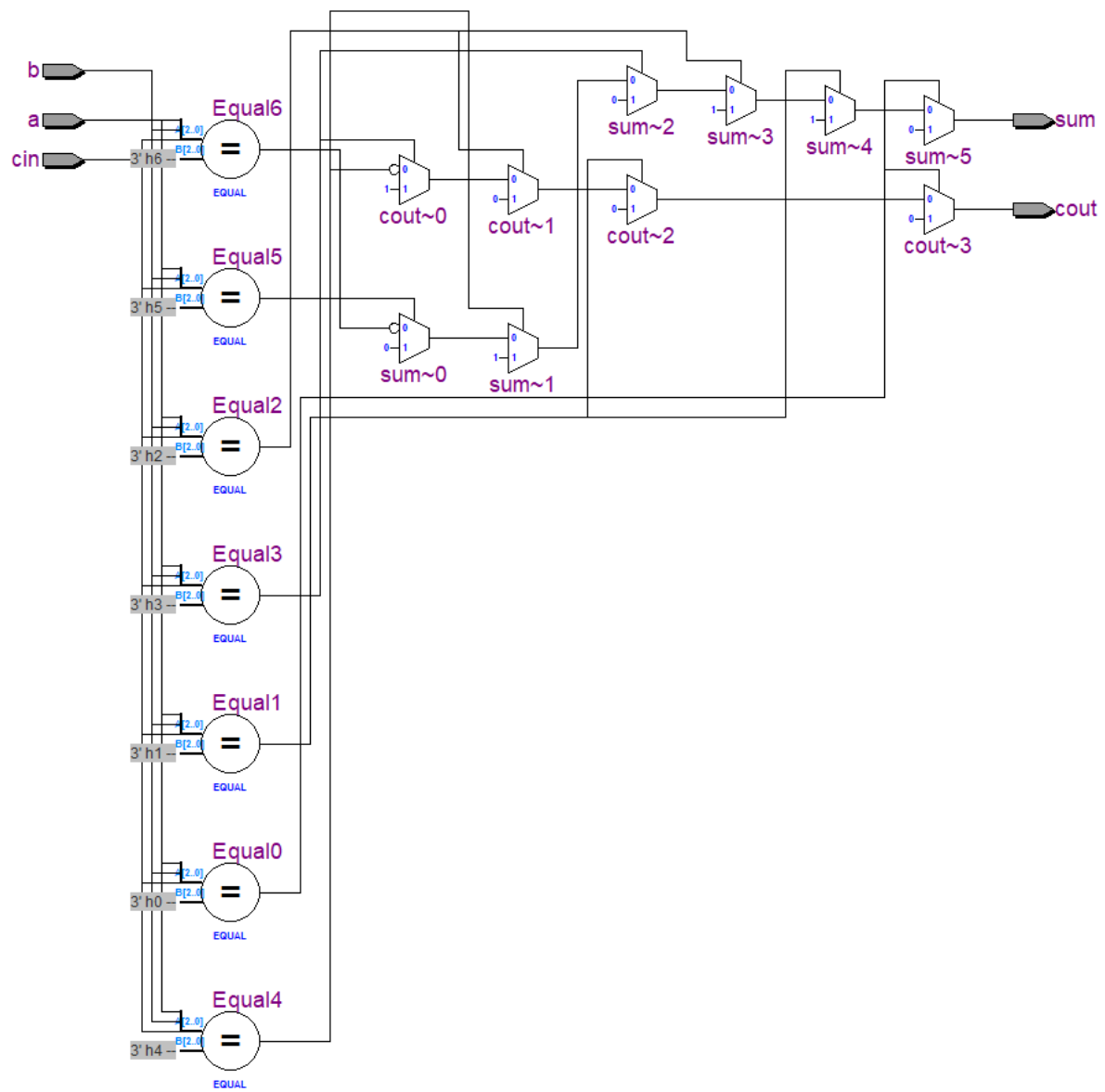Output 1)Cyclone II (RTL View), 2) Cyclone II (TTL View)




Q4 . Repeat the experiment execution flow for 4x1 multiplexer.

Code



```
module sneh20(
    input wire [3:0] data,
    input wire [1:0] sel,
    output reg out
);

always @(*) begin
    case(sel)
        2'b00: out = data[0];
        2'b01: out = data[1];
        2'b10: out = data[2];
        2'b11: out = data[3];
        default: out = 0;
    endcase
end

endmodule
```

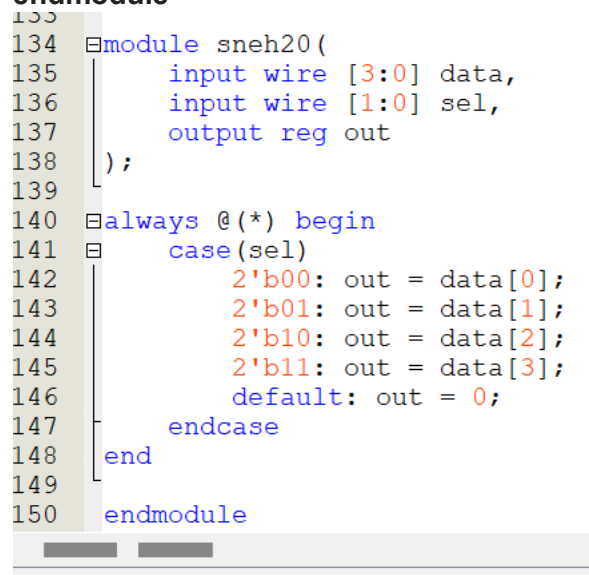

  Output 1)Cyclone II (RTL View), 2) Cyclone II (TTL View)



Q5 . Repeat the experiment execution flow for 2x4 Decoder.

Code

```

module sneh20(
    input wire [1:0] input_code,
    output reg [3:0] output_code
);

always @(*) begin
    case(input_code)
        2'b00: output_code = 4'b0001;
        2'b01: output_code = 4'b0010;
        2'b10: output_code = 4'b0100;
        2'b11: output_code = 4'b1000;
        default: output_code = 4'bxxxx;
    endcase
end

endmodule



```

```

152 module sneh20(
153     input wire [1:0] input_code,
154     output reg [3:0] output_code
155 );
156
157 always @(*) begin
158     case(input_code)
159         2'b00: output_code = 4'b0001;
160         2'b01: output_code = 4'b0010;
161         2'b10: output_code = 4'b0100;
162         2'b11: output_code = 4'b1000;
163         default: output_code = 4'bxxxx;
164     endcase
165 end
166
167 endmodule
168

```

  Output 1)Cyclone II (RTL View), 2) Cyclone II (TTL View)



Conclusion :-In this experiment we learnt that IF statements are synthesized by generating a multiplexer for each variable assigned within the if statement .We also

learnt to implement different logic circuits using the behavioural style of modelling and we got to know that the behavioural modelling is the fastest among all the other modelling styles .