

22bec121

Experiment – 7

Date:-7/3/2024

Lab Work

Q1 .To design a and implement a 8 x 8 RAM on FPGA .

Code (RAM)

```
module sneh67 (  
    input [5:0]address ,  
    input enable ,  
    input clk ,  
    input rw ,  
    output reg [7:0]data    //inout  
);  
  
reg [7:0]memory[7:0] ;  
integer i ;  
  
initial  
    begin  
        for (i = 0; i < 8; i = i + 1) begin  
            memory[i] = i ;  
        end  
    end  
  
always @(posedge clk)  
    begin  
        if (enable == 1)  
            begin  
                data = 0 ;  
            end  
    end
```

```
else
    begin
        if (rw == 0) //Read
            begin
                data <= memory[address] ;
            end
        else if (rw == 1) //Write
            begin
                memory[address] <= data ;
            end
        end
    end
end
endmodule
```

Quartus II 64-Bit - D:/22bec121/sneh67 - sneh67

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

sneh67

Project Navigator

Entity

Cyclone II: EP2C35F672C6

sneh67

Compilation Report - sneh67

sneh67.v

```

1 module sneh67 (
2     input [5:0]address ,
3     input enable ,
4     input clk ,
5     input rw ,
6     output reg [7:0]data    //inout
7 ) ;
8
9 reg [7:0]memory[7:0] ;
10 integer i ;
11
12 initial
13 begin
14     for (i = 0; i < 8; i = i + 1) begin
15         memory[i] = i ;
16     end
17 end
18
19 always @(posedge clk)
20 begin
21     if (enable == 1)
22     begin
23         data = 0 ;
24     end
25 else
26     begin
27         if (rw == 0) //Read
28         begin
29             data <= memory[address] ;
30         end
31         else if (rw == 1) //Write

```

Tasks

Flow: Compilation Customize...

Task

- ✓ Compile Design
- ✓ Analysis & Synthesis
- Edit Settings
- View Report
- ✓ Analysis & Elaboration
- Partition Merge
- Netlist Viewers
- RTL Viewer
- State Machine Viewer

Messages

All

Command: quartus_rpp sneh67 -c sneh67 --netlist_type=atom_map

Quartus II 64-Bit Netlist Viewers Preprocess was successful. 0 errors, 0 warnings

System (4) Processing (107)

100% 00:00:01

Quartus II 64-Bit - D:/22bec121/sneh67 - sneh67

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

sneh67

Project Navigator

Entity

Cyclone II: EP2C35F672C6

sneh67

Compilation Report - sneh67

sneh67.v

```
8
9  reg [7:0]memory[7:0] ;
10 integer i ;
11
12 initial
13 begin
14   for (i = 0; i < 8; i = i + 1) begin
15     memory[i] = i ;
16   end
17 end
18
19 always @(posedge clk)
20 begin
21   if (enable == 1)
22   begin
23     data = 0 ;
24   end
25 else
26   begin
27     if (rw == 0) //Read
28     begin
29       data <= memory[address] ;
30     end
31     else if (rw == 1) //Write
32     begin
33       memory[address] <= data ;
34     end
35   end
36 end
37 endmodule
38
```

Hierarchy Files Design

Tasks

Flow: Compilation Customize...

Task

- ✓ Compile Design
- ✓ Analysis & Synthesis
 - Edit Settings
 - View Report
- ✓ Analysis & Elaboration
 - Partition Merge
- Netlist Viewers
 - RTL Viewer
 - State Machine Viewer

All Messages

Message

Command: quartus_rpp sneh67 -c sneh67 --netlist_type=atom_map

Quartus II 64-Bit Netlist Viewers Preprocess was successful. 0 errors, 0 warnings

System (4) Processing (107)

100% 00:00:01


RTL Viewer - D:/22bec121/sneh67 - sneh67

File Edit View Tools Window Help


Search altera.com

Page Title: Display content Page: 1 of 1

sneh67:1

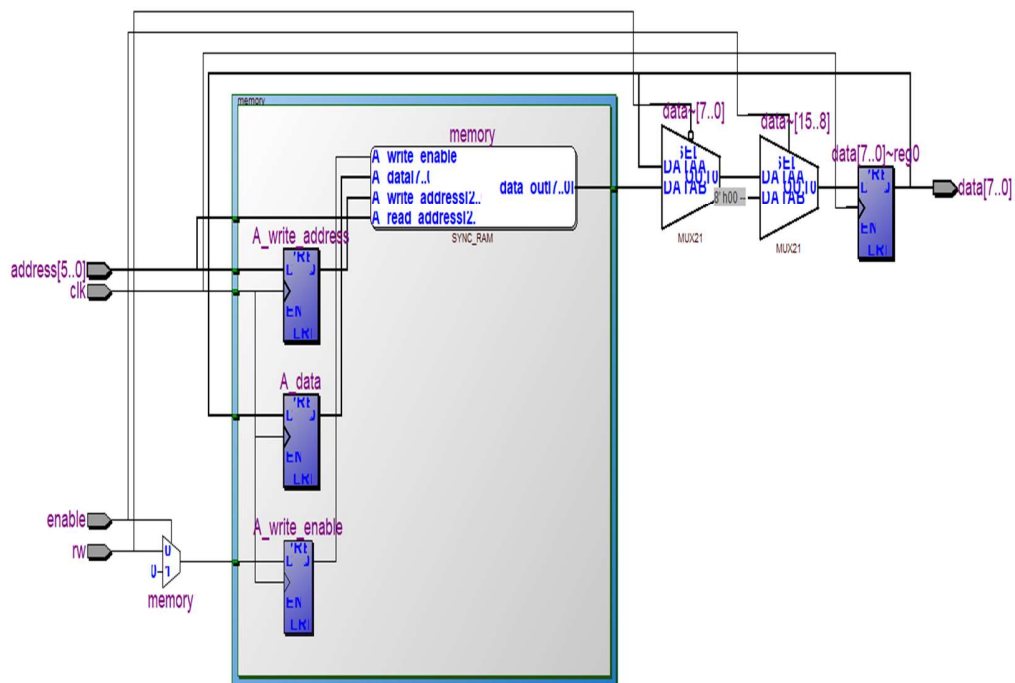


2)Cyclone II (TTL View)

 

Simulation Results :-

Read

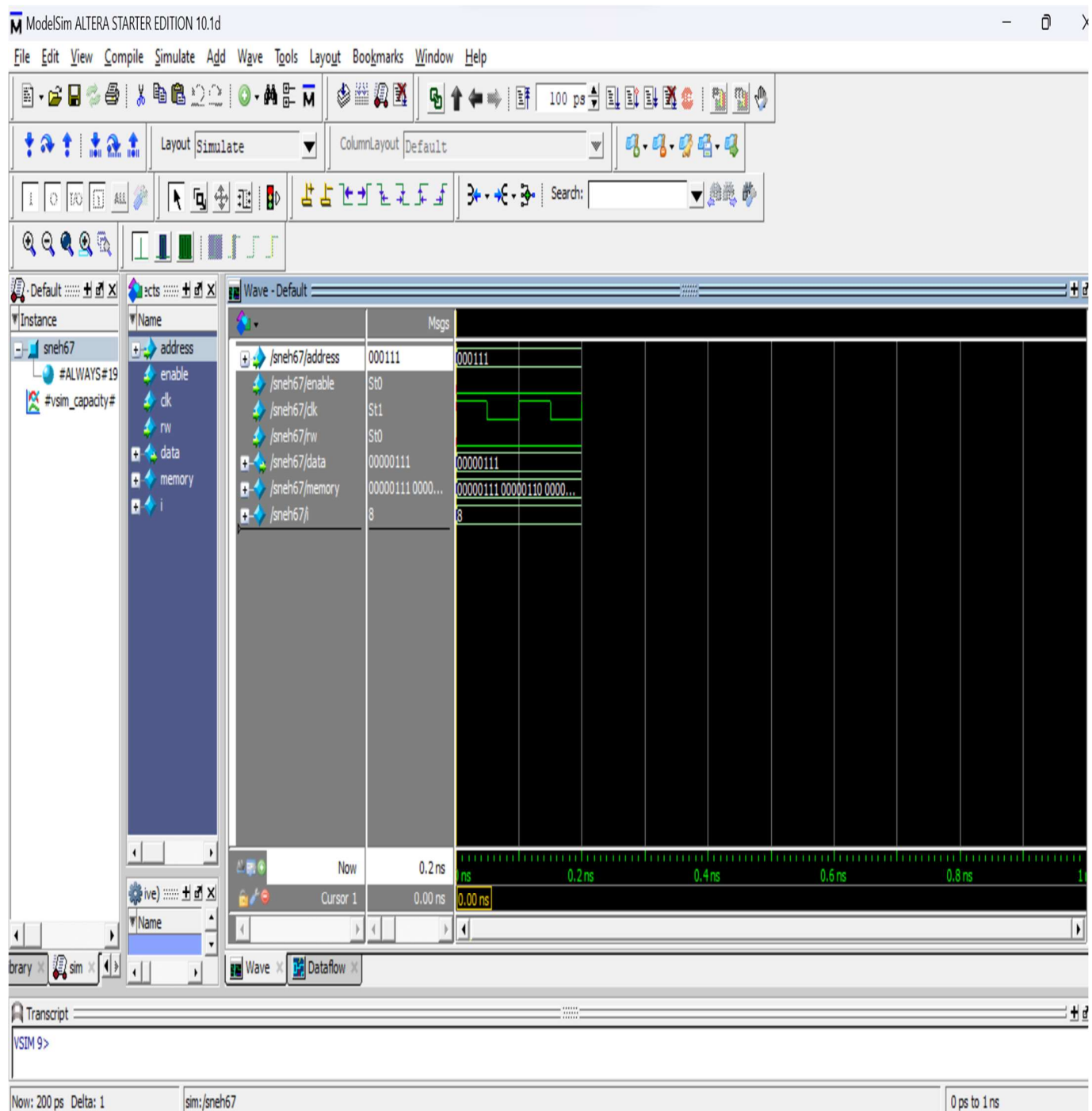

Write

ModelSim ALTERA STARTER EDITION 10.1d

File Edit View Compile Simulate Add Wave Tools Layout Bookmarks Window Help

100 ps

Layout Simulate ColumnLayout Default

Search:

Instance

- sneh67
 - #ALWAYS#19
 - #vsim_capacity#
 - address
 - enable
 - clk
 - rw
 - data
 - memory
 - i

Wave - Default

Msgs	
/sneh67/address	000111
/sneh67/enable	St0
/sneh67/clk	St1
/sneh67/rw	St1
/sneh67/data	01010101
/sneh67/memory	01010101 0000...
/sneh67/i	8

Now 0.7 ns

Cursor 1 0.00 ns

0 ns 0.2 ns 0.4 ns 0.6 ns 0.8 ns 1 ns

Transcript

VSIM 14>

Now: 700 ps Delta: 1 enable 0 ps to 1 ns

Conclusion :- In this experiment we learnt to design a 8 x 8 RAM and the concepts of RAM in depth .

We also learnt that what is the RTL and TTL of a RAM and also verified it using the Simulation .

We also found what problem occurs if we use inout declaration for data (it shows work file empty during simulation) ,

So we use output declaration and it still works same as a RAM performing both Read and Write Operation.

We also implemented RAM on a FPGA Kit . Also , we learned the different types of RAM used in Day – to – Day Scenarios .