

22bec121

Experiment – 1

Date:-11/1/2024

Lab Work

Q1 . Prepare all the basic gates using Data Flow Modelling. Observe the RTL and TTL design. Are they same? Change the chip and observe again and comment.

Code

```
// Basic Gates using DataFlow Modelling
```

```
/*
```

```
module sneh1(
```

```
input x,
```

```
input y,
```

```
output z1,    // XOR Gate
```

```
output z2,    // NOR Gate
```

```
output z3,    // XNOR Gate
```

```
output z4,    // NAND Gate
```

```
output z5,    // NOT Gate
```

```
output z6,    // OR Gate
```

```
output z7     // AND Gate
```

```
);
```

```
assign z1 = x^y ;
```

```
assign z2 = ~(x|y) ;
```

```
assign z3 = ~(x^y) ;
```

```
assign z4 = ~(x&y) ;
```

```
assign z5 = ~y ;
```

```
assign z6 = x|y ;
```

```
assign z7 = x&y ;
```

```
endmodule
```



```


1 // Basic Gates using DataFlow Modelling
2
3 module snehl(
4     input x,
5     input y,
6     output z1,      // XOR Gate
7     output z2,      // NOR Gate
8     output z3,      // XNOR Gate
9     output z4,      // NAND Gate
10    output z5,      // NOT Gate
11    output z6,      // OR Gate
12    output z7       // AND Gate
13 );
14
15     assign z1 = x^y ;
16     assign z2 = ~(x|y) ;
17     assign z3 = ~(x^y) ;
18     assign z4 = ~(x&y) ;
19     assign z5 = ~y ;
20     assign z6 = x|y ;
21     assign z7 = x&y ;
22
23 endmodule
24
25
26
27

```

Output

  1) Cyclone II (RTL View), 2) Cyclone II (TTL View), 3) Cyclone III (TTL View)



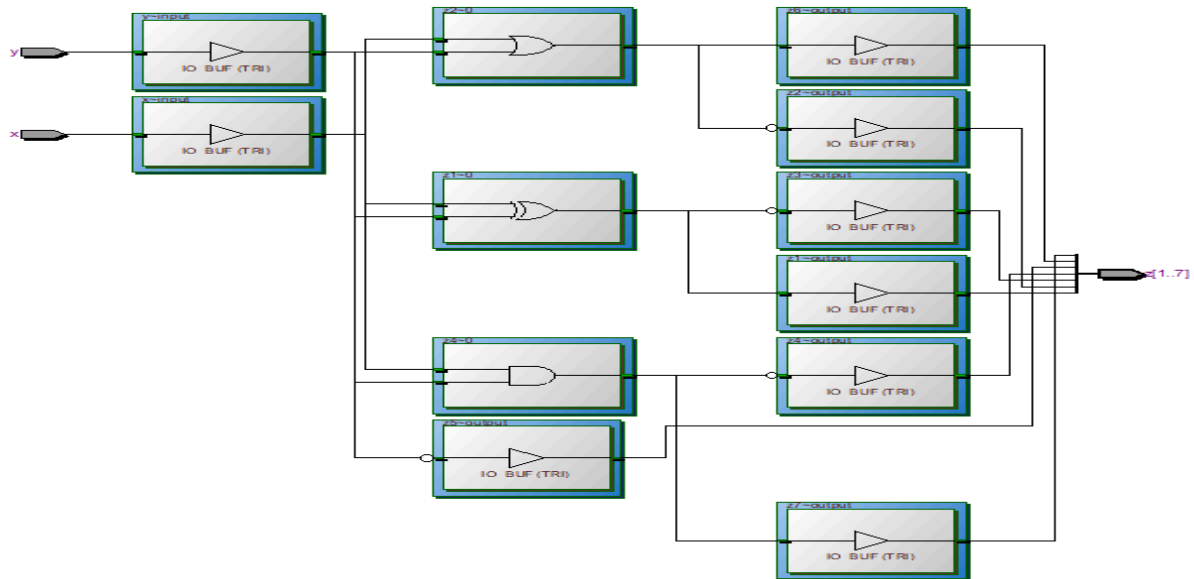

Q2 . Prepare all the basic gates using Behavioural Modelling. Observe the RTL and TTL design. Are they same? Compare the RTL and TTL obtained with the RTL and TTL obtained in Data Flow style of Modelling. Do you see any difference?

Code

//Basic Gates using Behavioral Modelling

```
module sneh1(
input x,
input y,
output reg z1, // XOR Gate
output reg z2, // NOR Gate
output reg z3, // XNOR Gate
output reg z4, // NAND Gate
output reg z5, // NOT Gate
output reg z6, // OR Gate
output reg z7 // AND Gate
);
```

```
always @*
begin
```

```

if (x==y)
begin
z1 = 0;
z3 = 1;
end
else if (x==0 && y==0)
begin
z2 = 1;
z6 = 0;
end
else if (x==1 && y==1)
begin
z4 = 0;
z7 = 1;
end
else
begin
z1 = 1;
z2 = 0;
z3 = 0;
z4 = 1;
z5 = ~y;
z6 = 1;
z7 = 0;
end
end
endmodule

```

```

25 //Basic Gates using Behavioral Modelling
26
27 module snehl(
28     input x,
29     input y,
30     output reg z1,        // XOR Gate
31     output reg z2,        // NOR Gate
32     output reg z3,        // XNOR Gate
33     output reg z4,        // NAND Gate
34     output reg z5,        // NOT Gate
35     output reg z6,        // OR Gate
36     output reg z7        // AND Gate
37 );
38
39 always @*
40 begin
41     if (x==y)
42     begin
43         z1 = 0;
44         z3 = 1;
45     end
46     else if (x==0 && y==0)
47     begin
48         z2 = 1;
49         z6 = 0;
50     end

```

```

51
52
53
54
55
56
57
58
59
60
61
62
63
64
65
66
67
68
69
70

```


```


else if (x==1 && y==1)
begin
    z4 = 0;
    z7 = 1;
end
else
begin
    z1 = 1;
    z2 = 0;
    z3 = 0;
    z4 = 1;
    z5 = ~y;
    z6 = 1;
    z7 = 0;
end
end
endmodule

```

Output

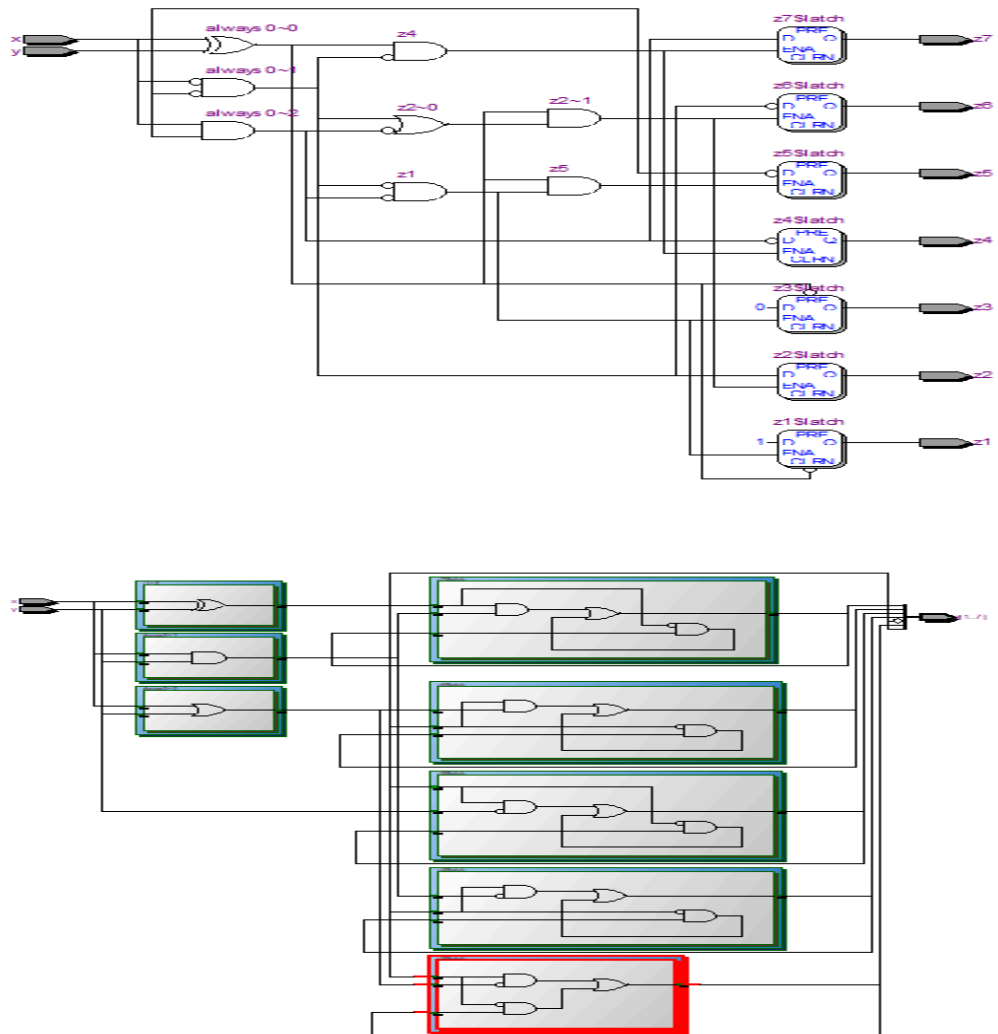1) Cyclone II (RTL View), 2) Cyclone II (TTL View), 3) Cyclone III (TTL View)



 

Q3 . Prepare XOR and XNOR gates using Structural Style of Modelling. Observe the RTL and TTL design. Are they same? Compare the RTL and TTL obtained with the RTL and TTL obtained in Data Flow style of Modelling and behaviour modelling. Do you see any difference?

//XOR and XNOR Gates using Structural Modelling

```
module not1(
input x,
output z
);
```

```
assign z = ~x;
```

```
endmodule
module and1(
input x,
input y,
output z
);
```

```
assign z = x&y;
```

```
endmodule
module or1(
input x,
input y,
```

```
output z  
);
```

```
assign z = x|y;  
endmodule  
module sneh1(  
input x,  
input y,  
output z1,    // XOR Gate  
output z2     // XNOR Gate  
);
```




```
wire p,q,r,s;  
not1 g1(x,p);  
and1 g2(p,y,q);  
not1 g3(y,r);  
and1 g4(x,r,s);  
or1 g5(q,s,z1);  
not1 g6(z1,z2);  
endmodule
```

```
69 //XOR and XNOR Gates using Structural Modelling  
70 module not1(  
71     input x,  
72     output z  
73 );  
74  
75     assign z = ~x;  
76 endmodule  
77 module and1(  
78     input x,  
79     input y,  
80     output z  
81 );  
82  
83     assign z = x&y;  
84 endmodule  
85 module or1(  
86     input x,  
87     input y,  
88     output z  
89 );  
90
```

```
90  
91     assign z = x|y;  
92 endmodule  
93 module sneh1(  
94     input x,  
95     input y,  
96     output z1,    // XOR Gate  
97     output z2     // XNOR Gate  
98 );  
99  
100     wire p,q,r,s;  
101     not1 g1(x,p);  
102     and1 g2(p,y,q);  
103     not1 g3(y,r);  
104     and1 g4(x,r,s);  
105     or1 g5(q,s,z1);  
106     not1 g6(z1,z2);  
107 endmodule  
108
```

Output

   1) Cyclone II (RTL View), 2) Cyclone II (TTL View), 3) Cyclone III (TTL View)



Q4 . Repeat the above steps for Gate Level modelling for all the basic gates and comment.

Code

```
module sneh1(  
input x,  
input y,  
output z1,    // XOR Gate  
output z2,    // NOR Gate  
output z3,    // XNOR Gate  
output z4,    // NAND Gate  
output z5,    // NOT Gate  
output z6,    // OR Gate  
output z7     // AND Gate  
);
```




```
xor(z1,x,y);  
nor(z2,x,y);  
xnor(z3,x,y);  
nand(z4,x,y);  
not(z5,y);  
or(z6,x,y);  
and(z7,x,y);
```

```
endmodule
```

```
110 module sneh1(  
111     input x,  
112     input y,  
113     output z1,    // XOR Gate  
114     output z2,    // NOR Gate  
115     output z3,    // XNOR Gate  
116     output z4,    // NAND Gate  
117     output z5,    // NOT Gate  
118     output z6,    // OR Gate  
119     output z7     // AND Gate  
120 );  
121  
122     xor(z1,x,y);  
123     nor(z2,x,y);  
124     xnor(z3,x,y);  
125     nand(z4,x,y);  
126     not(z5,y);  
127     or(z6,x,y);  
128     and(z7,x,y);  
129  
130 endmodule  
131
```

Output

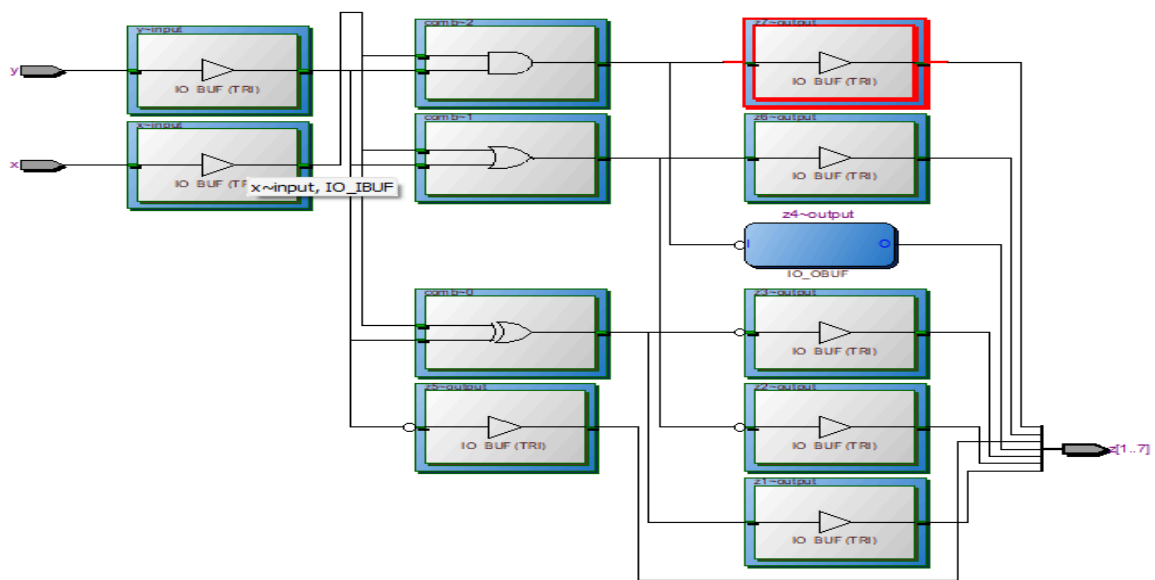  1) Cyclone II (RTL View), 2) Cyclone II (TTL View), 3) Cyclone III (TTL View)



Conclusion :- 1) Comments for Q₁ .

Here , the TTL view for both the Cyclone II and Cyclone III are different due to there internal hardware and the TTL View shows the available hardware to implement the given code .

2) Comments for Q₂ . , Q₃ . and Q₄ .

Here , the TTL View for both the Cyclone II and Cyclone III are different . In Cyclone III , the hardware includes the use of tri state buffers which are not available in the TTL View of Cyclone II Family .

3) In this experiment , we wrote the same logic using different Modelling Styles in Verilog and learnt about the difference that occurs in hardware for different Family of FPGA .